

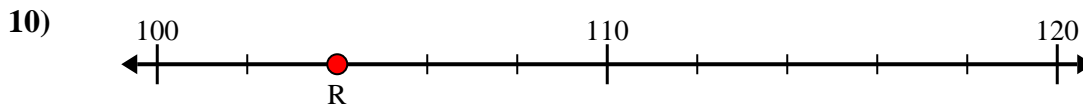
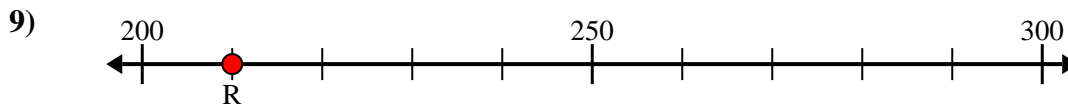
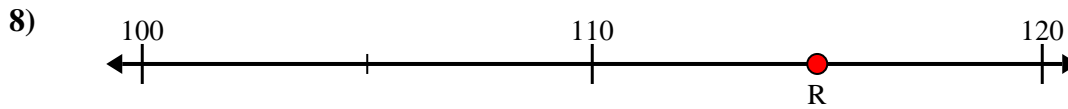
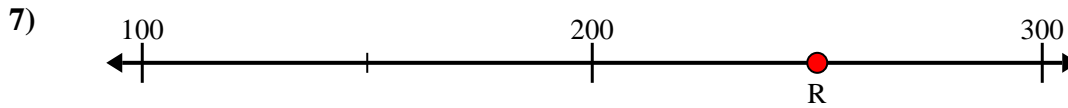
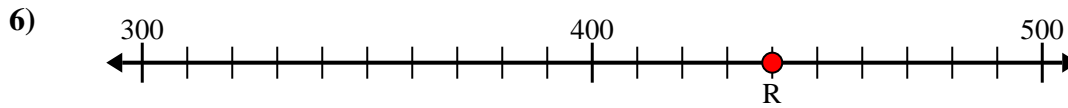
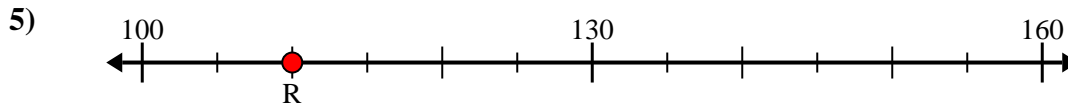
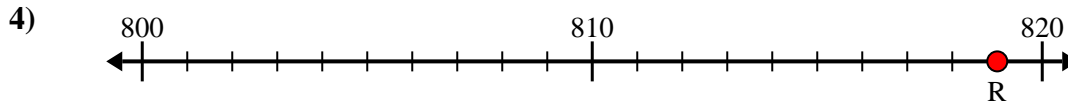
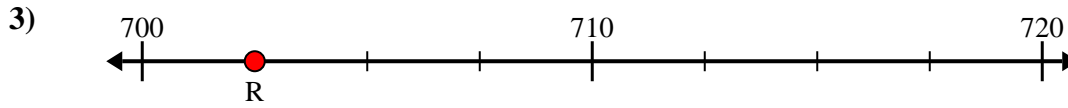


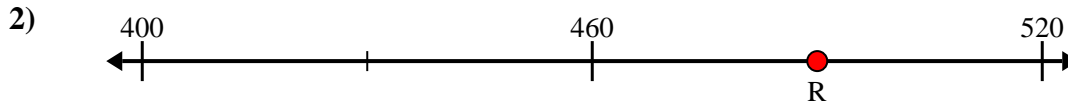

Trova il valore di R.










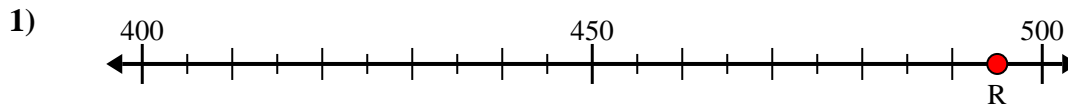


Risposte

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Trova il valore di R.

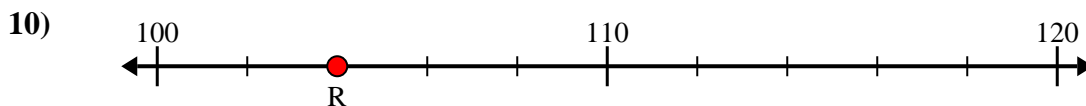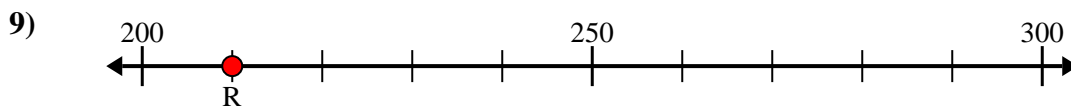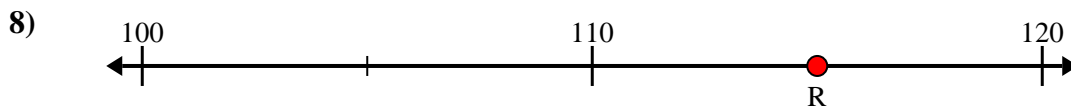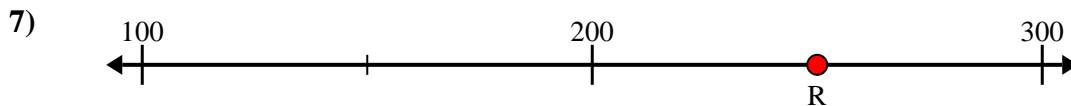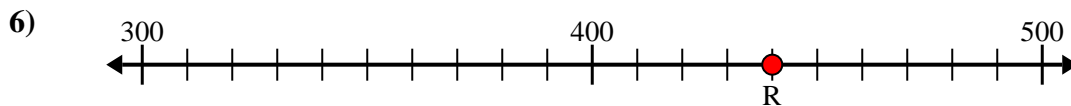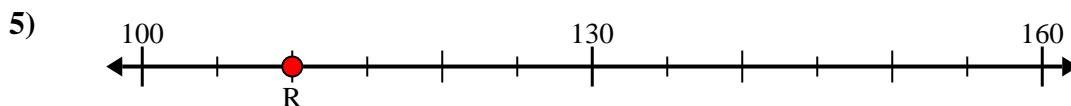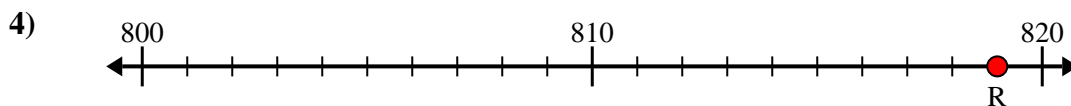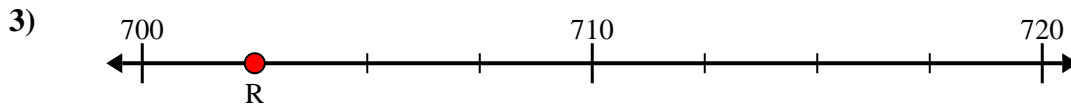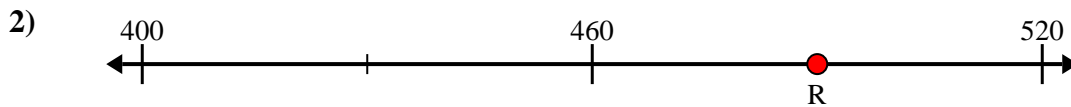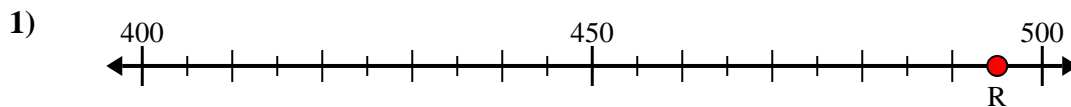

Risposte

1. 495

2. 490

3. 702,5

4. 819

5. 110

6. 440

7. 250

8. 115

9. 210

10. 104