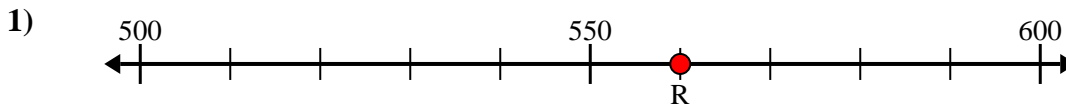





Trova il valore di R.


Risposte




1. _____

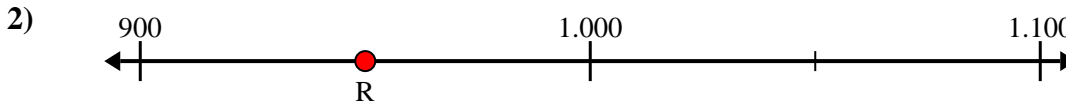


2. _____

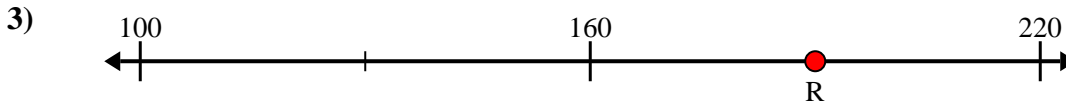


3. _____

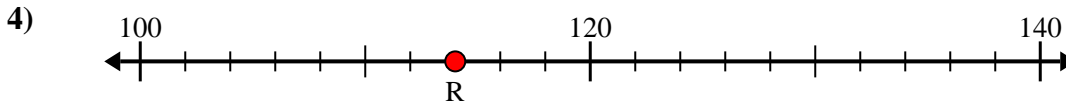


4. _____

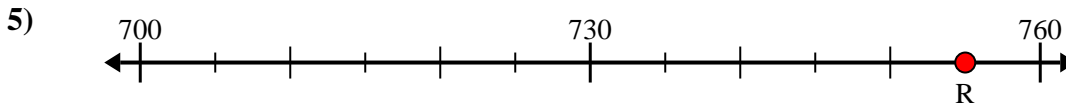


5. _____

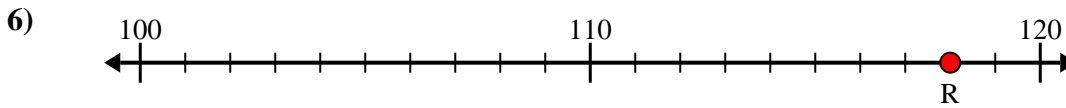


6. _____

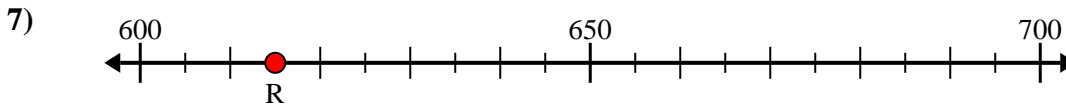


7. _____

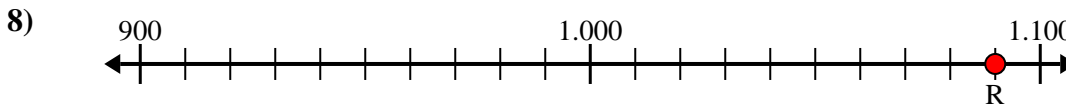

8. _____

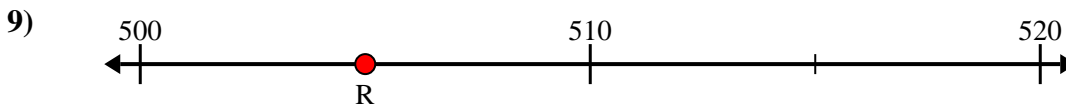











9. _____

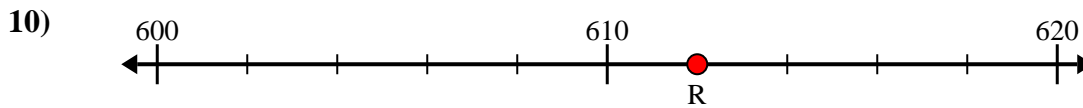

10. _____



Trova il valore di R.

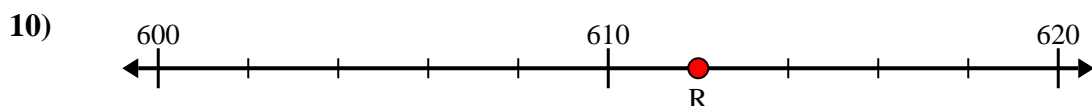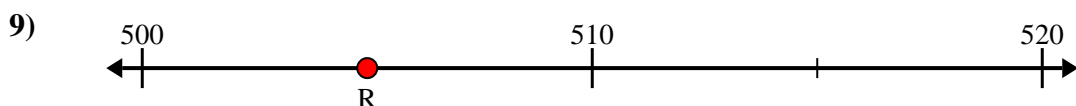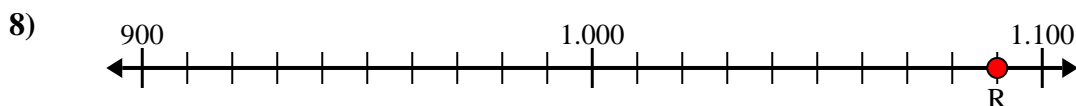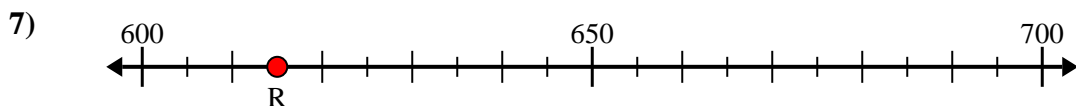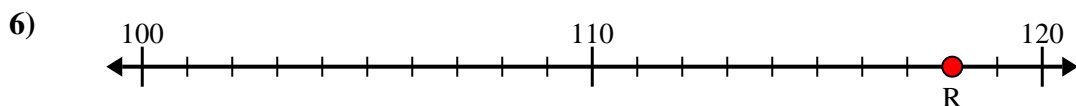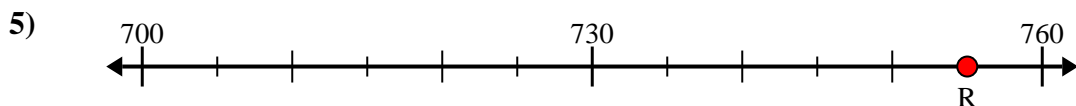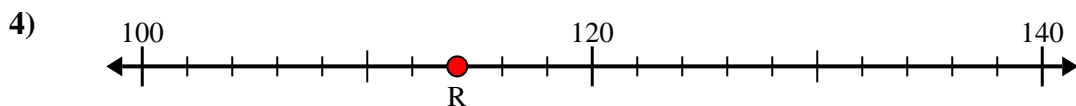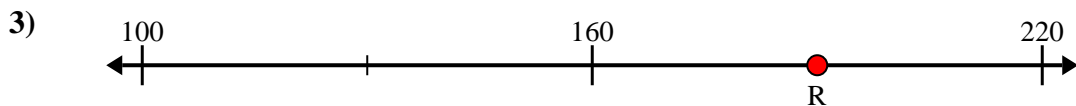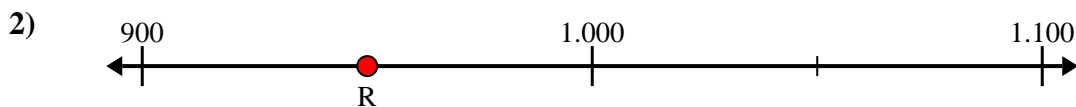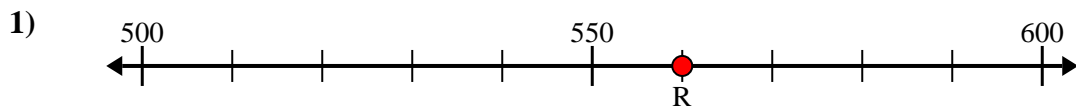

Risposte

1. 560

2. 950

3. 190

4. 114

5. 755

6. 118

7. 615

8. 1.090

9. 505

10. 612