

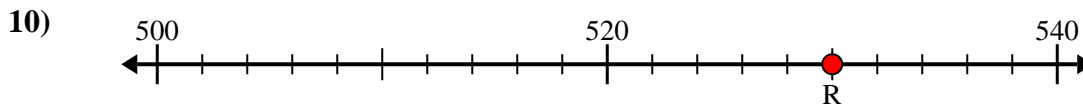
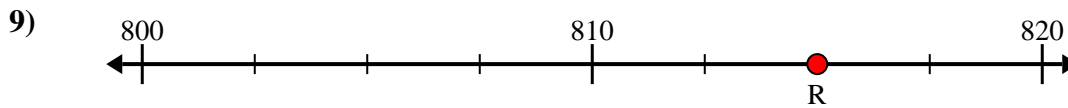
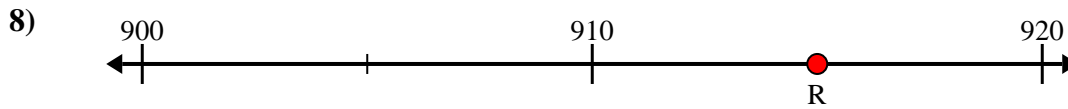
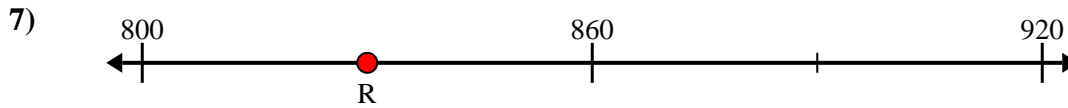
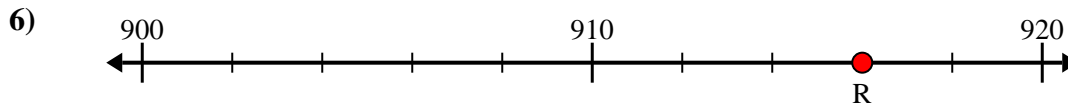
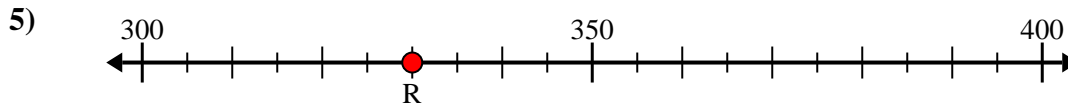
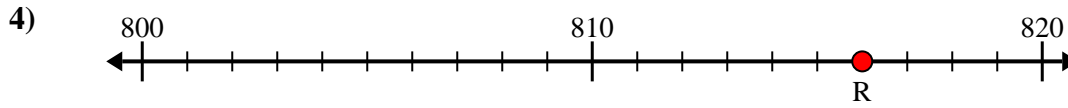
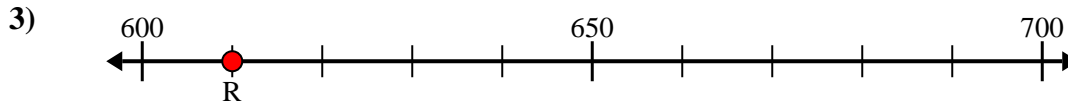


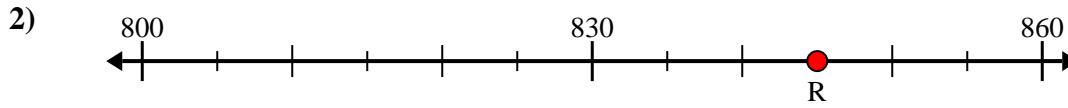

Trova il valore di R.










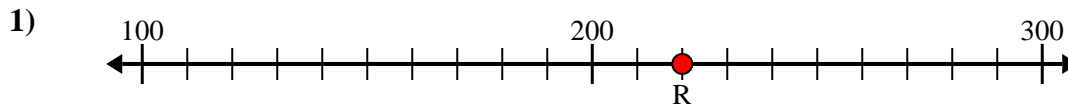


Risposte

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Trova il valore di R.

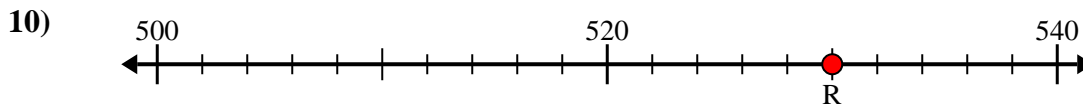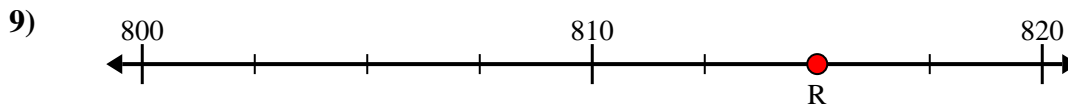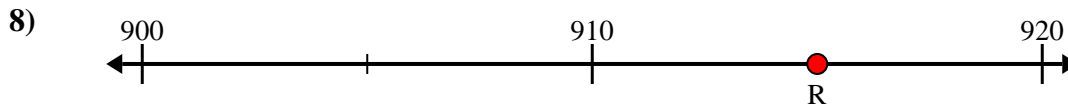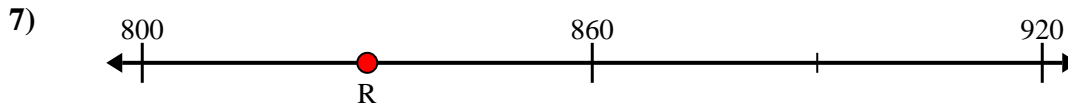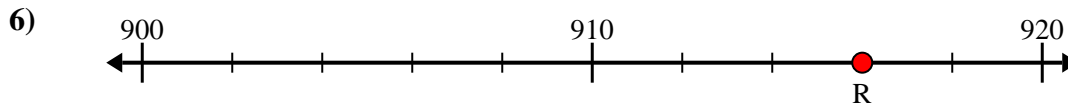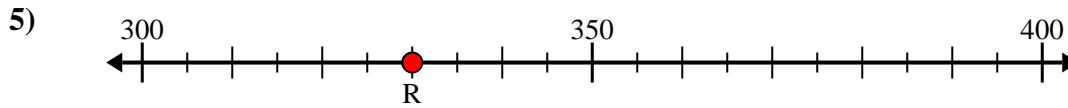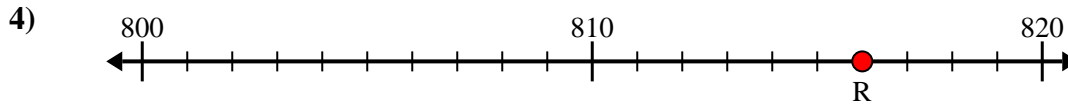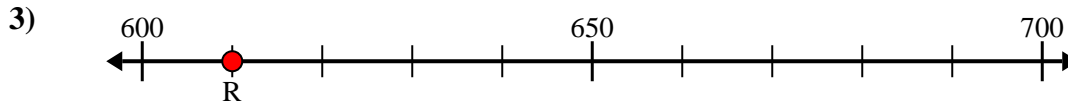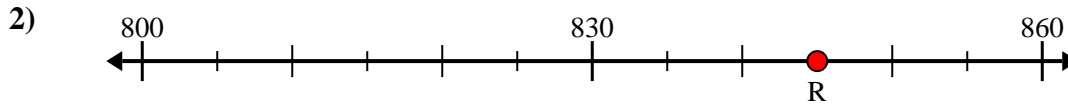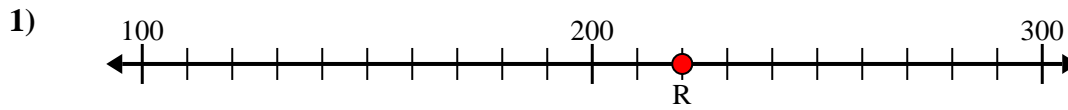

Risposte

1. 220

2. 845

3. 610

4. 816

5. 330

6. 916

7. 830

8. 915

9. 815

10. 530